



Nitish Kumar Gupta
Course: GATE
Computer Science Engineering(CS)

- HOME
- MY TEST
- BOOKMARKS
- MY PROFILE
- REPORTS
- BUY PACKAGE
- ASK AN EXPERT
- OFFER
- EXCLUSIVE OFFER FOR
OTS STUDENTS ONLY ON
BOOK PACKAGES

TOPICWISE : DIGITAL LOGIC-2 (GATE - 2019) - REPORTS

OVERALL ANALYSIS COMPARISON REPORT SOLUTION REPORT

ALL(17) CORRECT(7) INCORRECT(2) SKIPPED(8)

Q. 1

The race around condition occurs in a level trigger J-K flip-flop when

[Solution Video](#) | [Have any Doubt ?](#)

A Both the inputs are 0 Your answer is Wrong

B Both the inputs are 1 Correct Option

Solution :

(b)

In J-K flip-flop

J	K	Output
1	0	Set
0	1	Reset
0	0	Hold
1	1	Race around


C J = 1 and K = 0

D J = 0 and K = 1

[QUESTION ANALYTICS](#)

Q. 2

The circuit shown in figure below is:

 

[FAQ](#) [Solution Video](#) | [Have any Doubt ?](#)

A a MOD-2 counter

B a MOD-3 counter Your answer is Correct


Solution :

(b)

The truth table for the circuit is obtained below:

Present state		FF input		Next state	
Q_A	Q_B	T_A ($Q_A + Q_B$)	T_B ($\overline{Q_A} + Q_B$)	Q_A^+	Q_B^+
0	0	0	1	0	1
0	1	1	1	1	0
1	0	1	0	0	0
0	0	0	1	0	1

 So, the counter counts the sequence of 3 states as



Hence, the circuit is of a MOD-3 counter.

C Generate sequence 00, 10, 01, 00

D Generate sequence 00, 10, 00, 10, 00

[QUESTION ANALYTICS](#)

Q. 3

If Booth's Algorithm for multiplication is used then which of the following represents multiplier -29 in recorded form?

[Solution Video](#) | [Have any Doubt ?](#)

A 00 - 10 + 100 - 1

B 00 - 100 - 10 + 1

C 00 - 100 + 10 - 1 Your answer is Correct

Solution :

(c)

2's complement representation of -29 is 11100011.

1	0	-1
1	1	0
0	1	+1

0	0	0
0	0	0
1	0	-1
1	1	0
1	1	0

Recorded pair is : 00 – 100 + 10 – 1.


D 00 – 100 + 10 + 1

 QUESTION ANALYTICS



Q. 4

The representation of the value of 20 bit signed integer in 2's complement form is $P = (A72E5)_{16}$. Which of the following represents $16 \times P$ in 1's complement representation?

[FAQ](#) [Solution Video](#) [Have any Doubt ?](#) 

A $(72E4F)_{20}$

Correct Option

Solution :
(a)

$$\begin{aligned} P &= (A72E5)_{20} \\ &= 1010\ 0111\ 0010\ 1110\ 0101 \end{aligned}$$

$16 \times P$ means shift each bit 4 times left.
 $= 0111\ 0010\ 1110\ 0101\ 0000$

$16 \times P$ is in 2's complement form, so, to make 1's complement form “-1” will be added in result.
 $= 0\ 111\ 0010\ 1110\ 0101\ 0000$

$$\begin{array}{r} -1 \\ \hline 0111\ 0010\ 1110\ 0100\ 1111 \\ \hline \end{array}$$

$$= (72E4F)_{20}$$

B $(72E50)_{20}$

C $(72E4E)_{20}$


D None of the above

 QUESTION ANALYTICS



 
Q. 5

Amazon announce a new flip flop named Set-Reset-Toggle due to shortage elements to the electronics and computer industries. The device symbol and function table for this flip flop are shown below:



Which of the following is the characteristic equation?

[FAQ](#) [Solution Video](#) [Have any Doubt ?](#) 

A $Q^+ = TQ' + T'[Q(S \oplus R) + SR]$

B $Q^+ = (T \oplus Q) + S + R'Q$

C $Q^+ = T'Q + T[Q'(S + R) + SR]$

D $Q^+ = TQ' + T'[Q(S + R') + SR]$

Correct Option

Solution :
(d)

S	R	T	Q	Q ⁺
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

SR \ TQ	SR			
	00	01	11	10
00	0 4	12 8	1 9	
01	1 2	5 13	1 11	
11	3 7	15 10		
10	1 6	1 14	1 10	


$$\begin{aligned} Q^+ &= TQ' + T'QS + T'QR' + T'SR' \\ &= TQ' + T'[Q(S + R') + SR'] \end{aligned}$$

 QUESTION ANALYTICS



Q. 6

The minimum value of propagation delay in each Flip-Flop when a 10-bit ripple counter skip a count which is clocked at 10 MHz is _____ nsec.

[Solution Video](#) [Have any Doubt ?](#) 

10

Your answer is **Correct**10

Solution :
10

We know that for a stage change to ripple through n stages i.e. $T_C = n \times t_{pd}$.

$$f_c = \frac{1}{T_C}$$

$$f_c = \frac{1}{n \times t_{pd}}$$

So,
$$t_{pd} = \frac{1}{n \times f_c}$$


$$\begin{aligned} t_{pd}(\text{min}) &= \frac{1}{10 \times 10 \times 10^6 \text{ Hz}} \\ &= 0.01 \times 10^{-6} \text{ sec} \\ &= 10 \times 10^{-9} \text{ sec} \\ &= 10 \text{ nsec} \end{aligned}$$

 QUESTION ANALYTICS



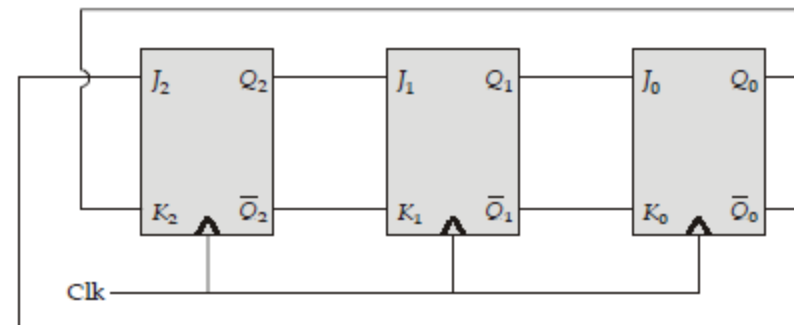Q. 7

Consider the counter circuit shown in the figure below:



The present state ($Q_2 Q_1 Q_0$) of the counter before applying the clock pulse was (101). If the input clock frequency to the circuit is 100 kHz, then the output frequency of the circuit will be _____ kHz.

[Solution Video](#) [Have any Doubt ?](#)

50

Correct Option

Solution :
50

Clock	Q_2	Q_1	Q_0
0	1	0	1
1	0	1	0
2	1	0	1

Hence, the sequence repeats itself after 2 clock pulses. Thus it is a divide by two counter.

$$\begin{aligned} \text{The output frequency} &= \frac{f_{in}}{2} \\ &= \frac{100}{2} \text{ kHz} = 50 \text{ kHz} \end{aligned}$$



Your Answer is 12.5


 QUESTION ANALYTICS



Q. 8

A synchronous counter is designed using J-K FF, X-Y FF and D-FF as shown below. X-Y FF truth table is

X	Y	Q_{n+1}
0	0	1
0	1	\bar{Q}_n
1	0	0
1	1	Q_n

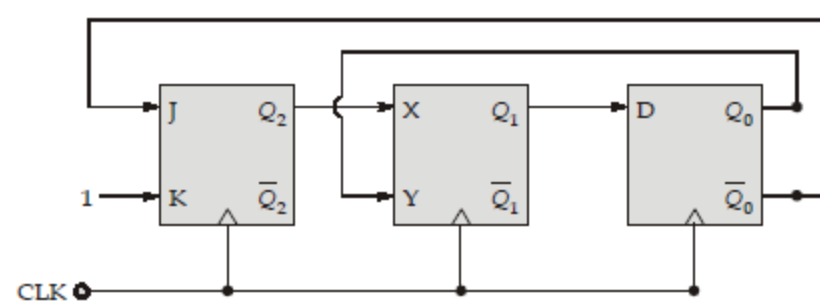

If the initial content of the counter is 001 at Q_2 , Q_1 , Q_0 , after the number of clock pulses counter is back to the same state is _____.

[Solution Video](#) [Have any Doubt ?](#)

4

Your answer is Correct4

Solution :
4

CLK	Q_2	Q_1	Q_0	FF2		FF1		FF0
				$J = \bar{Q}_0$	$K = 1$	$X = Q_2$	$Y = Q_0$	$D = Q_1$
	0	0	1	0	1	0	1	0
1	0	1	0	1	1	0	0	1
2	1	1	1	0	1	1	1	1
3	0	1	1	0	1	0	1	1
4	0	0	1					

∴ Counter is back to the initial state after 4 clock pulses.

 QUESTION ANALYTICS



Q. 9

The difference between 201 and next larger double precision number is 2^P , if IEEE double precision format is used then the value of P is _____.

[FAQ](#) [Solution Video](#) [Have any Doubt ?](#)

Solution :

-45

Format of IEEE double Precision:

Sign	Exponent	Mantissa
1 bit	11 bits	52 bits

Representation of 201 = $(1.1001001)_2 \times 2^7$

Next largest number = $(1.1001001)_2 \times 2^{-52}$

So, Difference = $2^{-52} \times 2^7$
 $= 2^{(-52+7)}$
 $= 2^{-45}$


Comparing with 2^P will gives $P = -45$.

QUESTION ANALYTICS



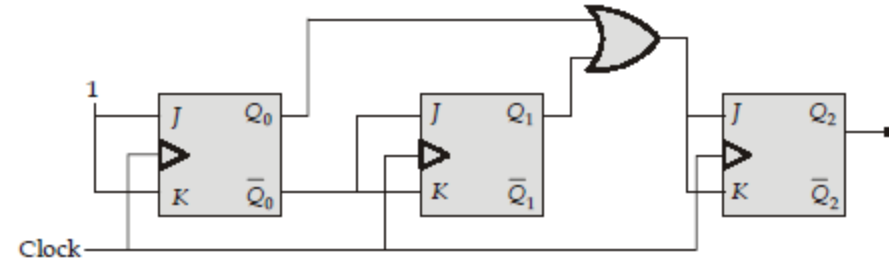Q. 10

Consider the circuit given below with initial state $Q_2Q_1Q_0 = 000$.



Which one of the following is the correct state sequence of the circuit?

FAQ [Solution Video](#) [Have any Doubt ?](#)

A 0, 6, 3, 4, 1, 7, 2, 5, 0

B 0, 3, 6, 1, 4, 7, 2, 5, 0

Correct Option

Solution :

(b)

$J = K = 1$	$J = K = \overline{Q_0}$	$J = K = Q_0 + Q_1$	
Q_0	Q_1	Q_2	
0	0	0	= 0
1	1	0	= 3
0	1	1	= 6
1	0	0	= 1
0	0	1	= 4
1	1	1	= 7
0	1	0	= 2
1	0	1	= 5
0	0	0	= 0

So, sequence must be 0, 3, 6, 1, 4, 7, 2, 5, 0.

C 0, 3, 6, 4, 1, 7, 2, 5, 0


D 0, 6, 3, 1, 4, 7, 2, 5, 0

QUESTION ANALYTICS



 Q. 11

Consider 8-bit left shift register and D flip-flop shown in figure below is synchronized with same clock. The D flip-flop is initially cleared.



Which of the following represents the behaviour of above circuit?

[Solution Video](#) [Have any Doubt ?](#)

A Binary to 2's complement converter

B Binary to 1's complement converter

C Binary to Excess-3 code converter

D Binary to Gray code converter

Your answer is **Correct**

Solution :

(d)

Output of ExOR Gate = $b_i \oplus b_{i+1}$

Initially $Q = 0$ assume

So, After 1 clock, $Z = b_7 \oplus b_0$
 After 2 clock, $Z = b_7 \oplus b_6$
 After 3 clock, $Z = b_6 \oplus b_5$
 After 4 clock, $Z = b_5 \oplus b_4$
 After 5 clock, $Z = b_4 \oplus b_3$
 After 6 clock, $Z = b_3 \oplus b_2$
 After 7 clock, $Z = b_2 \oplus b_1$
 After 8 clock, $Z = b_1 \oplus b_0$


Which is same as Binary to gray code converter.

QUESTION ANALYTICS



 Q. 12

Consider the circuit shown in the figure below:



The value of output $Q_0Q_1Q_2$ and the value of output Y after the 5th clock pulse is
(Assume that initially all the flip-flop are in reset state)

[FAQ](#) [Solution Video](#) [Have any Doubt ?](#)

A Output = 001 and $Y = 1$

B Output = 101 and $Y = 0$

Correct Option

Solution :

(b)

The given circuit represents a 3-bit counter. So the count can be represented as

Clk	Q_2	Q_1	Q_0
Initially	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

⇒ 5th clock pulse

∴ $Y = Q_2 \oplus Q_1 \oplus Q_0$
 $= 1 \oplus 0 \oplus 1 = 0$

C Output = 100 and $Y = 1$


D Output = 010 and $Y = 1$

[QUESTION ANALYTICS](#)



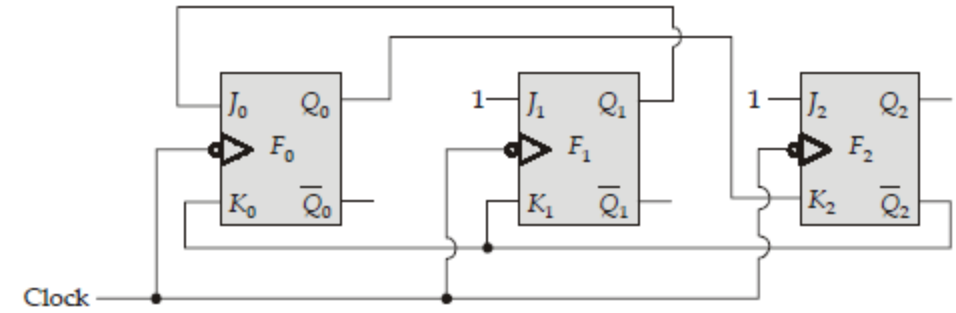Q. 13

Consider the counter circuit shown in the figure below:



The counter is designed such that it counts the states 3 → 4 → 6 → 7, then which of the following statements about this counter is true?

[FAQ](#) [Solution Video](#) [Have any Doubt ?](#)

A The counter enters into a lockout state if the counter starts from $(5)_{10}$

B The counter enters into a lockout state if the counter starts from $(2)_{10}$

C The counter enters into a lockout state if the counter starts from $(3)_{10}$

D The counter do not enters into a lockout state


Correct Option

Solution :

(d)

Test for Lockout

Present State			Present Input						Next State		
Q_2	Q_1	Q_0	J_2	K_2	J_1	K_1	J_0	K_0	Q_2	Q_1	Q_0
0	0	0	1	0	1	1	0	1	1	1	0
0	0	1	1	1	1	1	0	1	1	1	0
0	1	0	1	0	1	1	1	1	1	0	1
1	0	1	1	1	1	0	0	0	0	1	1

 


Hence, the counter does not enter into lockout state.


[QUESTION ANALYTICS](#)



Q. 14

Consider Register R shown below:

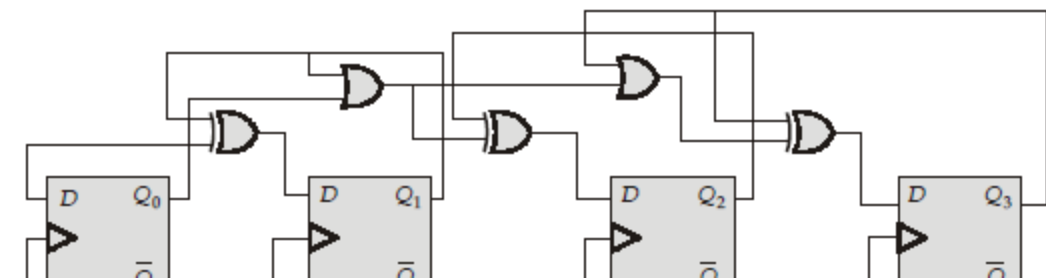

 

Clock— Consider $X = x_3 x_2 x_1 x_0$ denote the contents of register R as a two's complement number. What is the contents of Register R after two clock ticks?

[FAQ](#) [Solution Video](#) [Have any Doubt ?](#)

A X
Correct Option

Solution :

(a)

After 1st clock tick:

$$x_0^+ = x_0$$

$$x_1^+ = x_0 \oplus x_1$$

$$x_2^+ = (x_0 + x_1) \oplus x_2$$

$$x_3^+ = (x_0 + x_1 + x_2) \oplus x_3$$

After 2nd clock tick:

$$(x_0^+)^+ = x_0^+ = x_0$$

$$(x_1^+)^+ = x_0^+ \oplus x_1^+ = x_0 \oplus x_0 \oplus x_1 = 0 \oplus x_1 = x_1$$

$$(x_2^+)^+ = (x_0^+ + x_1^+) \oplus x_2^+ = (x_0 + (x_0 \oplus x_1)) \oplus (x_0 + x_1) \oplus x_2$$

$$= x_0 \oplus x_0 \oplus x_1 \oplus x_0 \oplus x_0 x_1 \oplus x_0 \oplus x_1 \oplus x_0 x_1 \oplus x_2$$

$$= x_2$$

$$(x_3^+)^+ = (x_0^+ + x_1^+ + x_2^+) \oplus x_3^+$$

$$= x_3 \text{ only}$$

So, after 2 clock tick Register R contain X only.

B X + 1

C X + 2

D X – 1

QUESTION ANALYTICS
+

Q. 15

Consider a binary counter is being pulsed by a 256 kHz clock signal. If the output frequency from the last flip-flop is 8 kHz, then the mod value of counter is _____.

[Solution Video](#) [Have any Doubt ?](#)

32
Your answer is **Correct**32

Solution :

32

We know that, for Mod-N counter $f_o = \frac{f_i}{N}$

$$f_o = \text{Output frequency} = 8 \text{ kHz}$$

$$f_i = \text{Input frequency} = 256 \text{ kHz}$$

$$\text{Mod N} = \frac{f_i}{f_o}$$

$$= \frac{256 \text{ kHz}}{8 \text{ kHz}} = 32$$

QUESTION ANALYTICS
+

Q. 16

The following bit pattern represents a floating point number in IEEE-754 single precision format:

1	10000101	110100000000000000000000
Sign	Exponent	Mantissa

The value of the number in decimal form is _____.

[Solution Video](#) [Have any Doubt ?](#)

-116
Correct Option

Solution :

-116

Exponent = 1000 0101 = 133

Biased exponent = Actual exponent + Bias

Actual exponent = Biased exponent – Bias

$$= 133 - 127 = 6$$

Mantissa = 110100000000000000000000

Number = 1.1101×2^6


$$= -1110100$$

$$= (-116)_{10}$$

QUESTION ANALYTICS
+

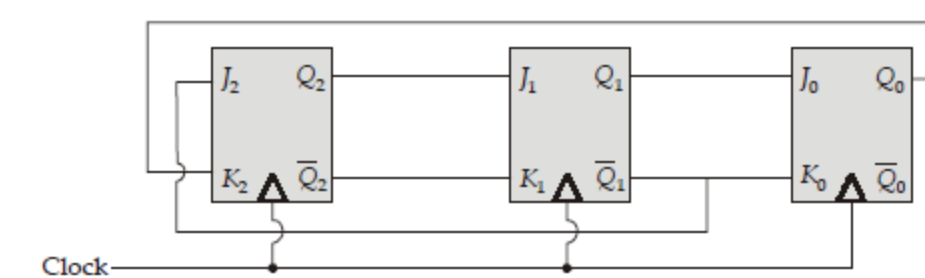Q. 17

Consider the circuit shown in the figure below:



Then the value of $(Q_2 Q_1 Q_0)$ after the first clock pulse is equal to _____ (Assume all the outputs to be '0' initially)

Then the value of $(Q_2Q_1Q_0)$ after the first clock pulse is equal to _____. (Assume all the outputs to be 0 initially)

[Solution Video](#) | [Have any Doubt ?](#)

100

Your answer is **Correct**100

Solution :

100

At first cycle, the inputs of flip-flop are

$$J_2K_2 = 1\ 0 \text{ (Set)}$$

$$J_1K_1 = 0\ 1 \text{ (Reset)}$$

$$J_0K_0 = 0\ 1 \text{ (Reset)}$$

$$\therefore Q_2 = 1$$

$$Q_1 = 0$$

$$Q_0 = 0$$

$$\therefore \text{Output } (Q_2Q_1Q_0) = (100)_2$$

 QUESTION ANALYTICS

+